

# Technical Information Switching diagrams

#### Switching diagrams 41200-41311

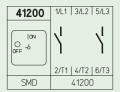
# $\textbf{Main/Emergency-Off Switches} \cdot \textbf{Main Switches} \cdot \textbf{ON-OFF Switches, 2 pole}$



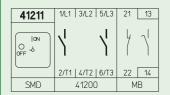
Switching programme 41200 2 pole without auxiliary contacts



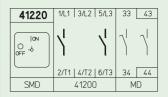
Switching programme 41211 2 pole with 2 auxiliary contacts 1 n/o late make/early break + 1 n/c



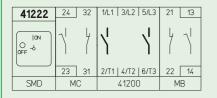
Switching programme 41220 2 pole with 2 auxiliary contacts 2 n/o late make/early break



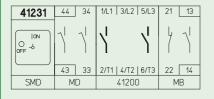Switching programme 41222 2 pole with 4 auxiliary contacts 2 n/o late make/early break + 2 n/c




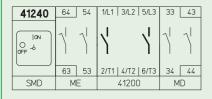Switching programme 41231 2 pole with 4 auxiliary contacts 3 n/o late make/early break + 1 n/c




Switching programme 41240 2 pole with 4 auxiliary contacts 4 n/o late make/early break
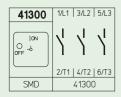
#### Main/Emergency-Off Switches · Main Switches · ON-OFF Switches, 3 pole



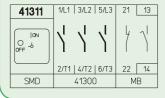Switching programme 41300 3 pole without auxiliary contacts




Switching programme 41311 3 pole with 2 auxiliary contacts 1 n/o late make/early break + 1 n/c




### **Technical Information** Switching diagrams

#### Switching diagrams 41320-41420

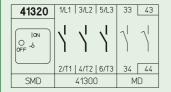
# $\textbf{Main/Emergency-Off Switches} \cdot \textbf{Main Switches} \cdot \textbf{ON-OFF Switches, 3 pole}$



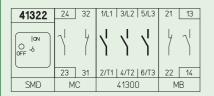
Switching programme 41320 3 pole with 2 auxiliary contacts 2 n/o late make/early break



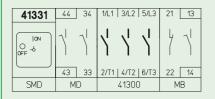Switching programme 41322 3 pole with 4 auxiliary contacts 2 n/o late make/early break + 2 n/c




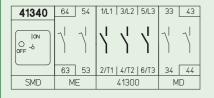Switching programme 41331 3 pole with 4 auxiliary contacts 3 n/o late make/early break + 1 n/c




Switching programme 41340 3 pole with 4 auxiliary contacts 4 n/o late make/early break

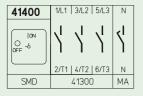
### Main/Emergency-Off Switches · Main Switches · ON-OFF Switches, 4 pole



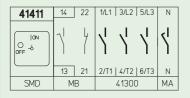Switching programme 41400 4 pole without auxiliary contacts Neutral contact early make/late break



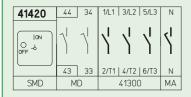Switching programme 41411 4 pole with 2 auxiliary contacts 1 n/o late make/early break + 1 n/c Neutral contact early make/late break




Switching programme 41420 4 pole with 2 auxiliary contacts 2 n/o late make/early break Neutral contact early make/late break


# Technical Information Switching diagrams

### Switching diagrams 41600-41800

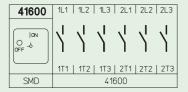
# $\textbf{Main/Emergency-Off Switches} \cdot \textbf{Main Switches} \cdot \textbf{ON-OFF Switches}, \textbf{6 pole}$



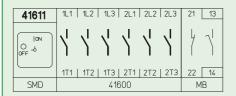
Switching programme 41600 6 pole without auxiliary contacts



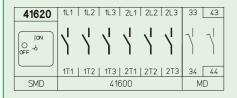
Switching programme 41611 6 pole with 2 auxiliary contacts 1 n/o late make/early break + 1 n/c



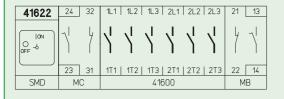
Switching programme 41620 6 pole with 2 auxiliary contacts 2 n/o late make/early break



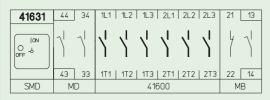Switching programme 41622 6 pole with 4 auxiliary contacts 2 n/o late make/early break + 2 n/c




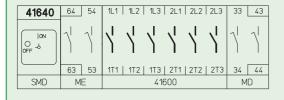Switching programme 41631 6 pole with 4 auxiliary contacts 3 n/o late make/early break + 1 n/c



Switching programme 41640 6 pole with 4 auxiliary contacts 4 n/o late make/early break

# **ON-OFF Switches, 8 pole**

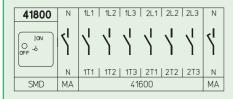


Switching programme 41800 8 pole without auxiliary contacts 2 neutral contacts early make/late break




### Technical Information Switching diagrams

### Switching diagrams 42400-42800

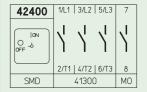
### $\textbf{Main/Emergency-Off Switches} \cdot \textbf{Main Switches} \cdot \textbf{ON-OFF Switches, with main contact module}$



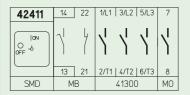
Switching programme 42400 4 pole without auxiliary contacts



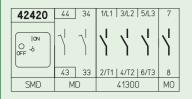
Switching programme 42411 4 pole with 2 auxiliary contacts 1 n/o late make/early break + 1 n/c



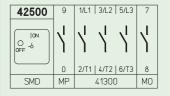
Switching programme 42420 4 pole with 2 auxiliary contacts 2 n/o late make/early break



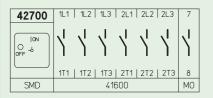
Switching programme 42500 5 pole without auxiliary contacts



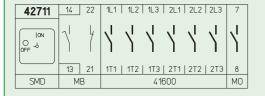
Switching programme 42700 7 pole without auxiliary contacts



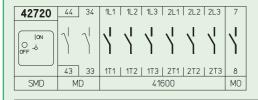Switching programme 42711 7 pole with 2 auxiliary contacts 1 n/o late make/early break + 1 n/c



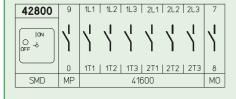Switching programme 42720 7 pole with 2 auxiliary contacts 2 n/o late make/early break




Switching programme 42800 8 pole without auxiliary contacts


# Technical Information Switching diagrams

### Switching diagrams 45300-47200

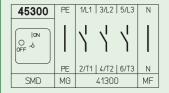
### Main/Emergency-Off Switches · Main Switches · ON-OFF Switches, with N and PE-terminal



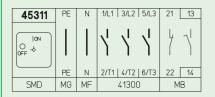Switching programme 45300 3 pole without auxiliary contacts with N and PE-terminal




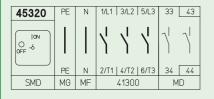Switching programme 45311 3 pole with 2 auxiliary contacts 1 n/o late make/early break + 1 n/c with N and PE-terminal




Switching programme 45320 3 pole with 2 auxiliary contacts 2 n/o late make/early break with N and PE-terminal

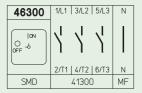
# $\textbf{Main/Emergency-Off Switches} \cdot \textbf{Main Switches} \cdot \textbf{ON-OFF Switches, with N-terminal}$



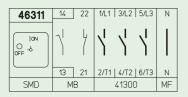Switching programme 46300 3 pole without auxiliary contacts with N-terminal




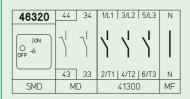Switching programme 46311 3 pole with 2 auxiliary contacts 1 n/o late make/early break + 1 n/c with N-terminal



Switching programme 46320 3 pole with 2 auxiliary contacts 2 n/o late make/early break with N-terminal
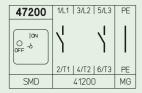
# Main/Emergency-Off Switches · Main Switches · ON-OFF Switches, with PE-terminal




Switching programme 47200 2 pole without auxiliary contacts with PE-terminal




### Technical Information Switching diagrams

#### Switching diagrams 47211-71200

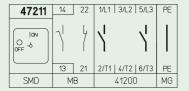
#### Main/Emergency-Off Switches · Main Switches · ON-OFF Switches, with PE-terminal



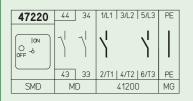
Switching programme 47211 2 pole with 2 auxiliary contacts 1 n/o late make/early break + 1 n/c with PE-terminal



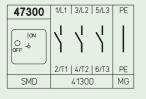
Switching programme 47220 2 pole with 2 auxiliary contacts 2 n/o late make/early break with PE-terminal



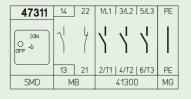
Switching programme 47300 3 pole without auxiliary contacts with PE-terminal



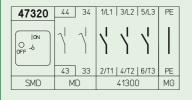
Switching programme 47311 3 pole with 2 auxiliary contacts 1 n/o late make/early break + 1 n/c with PE-terminal



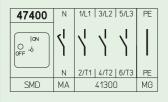Switching programme 47320 3 pole with 2 auxiliary contacts 2 n/o late make/early break with PE-terminal




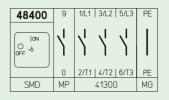Switching programme 47400 4 pole without auxiliary contacts Neutral contact early make/late break with PE-terminal



Switching programme 48400 4 pole without auxiliary contacts with PE-terminal

### Changeover Switches, 2 pole

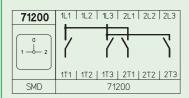

Switching programme 71200 2 pole without auxiliary contacts

# Technical Information Switching diagrams

#### Switching diagrams 71201-71222


#### Changeover Switches, 2 pole 1L1 | 1L2 | 1L3 | 2L1 | 2L2 | 2L3 Switching programme 71201 71201 2 pole with 2 auxiliary contacts 1 n/o late make/early break + 1 n/c in position 2 SMD 71200 1 1 1 1L2 1L3 2L1 2L2 2L3 Switching programme 71202 71202 2 pole with 2 auxiliary contacts 2 n/o late make/early break in position 2 SMD 71200 MD 1L1 1L2 1L3 2L1 2L2 2L3 Switching programme 71210 71210 14 22 2 pole with 2 auxiliary contacts 1 n/o late make/early break + 1 n/c in position 1 13 21 1T1 | 1T2 | 1T3 | 2T1 | 2T2 | 2T3 SMD MB 71200 1L1 | 1L2 | 1L3 | 2L1 | 2L2 | 2L3 Switching programme 71211 71211 2 pole with 4 auxiliary contacts 1 n/o late make/early break + 1 n/c in position 1 1 n/o late make/early break + 1 n/c in position 2 13 32 24 SMD MB 71200 MC 1L1 | 1L2 | 1L3 | 2L1 | 2L2 | 2L3 Switching programme 71212 22 33 43 71212 14 2 pole with 4 auxiliary contacts 1 n/o late make/early break + 1 n/c in position 1 2 n/o late make/early break in position 2 1T1 | 1T2 | 1T3 | 2T1 | 2T2 | 2T3 SMD MB 71200 Switching programme 71220 71220 44 34 11.1 11.2 11.3 21.1 21.2 21.3 2 pole with 2 auxiliary contacts 2 n/o late make/early break in position 1 1T1 | 1T2 | 1T3 | 2T1 | 2T2 | 2T3 SMD MD 71200 71221 44 34 1L1 1L2 1L3 2L1 2L2 2L3 Switching programme 71221 2 pole with 4 auxiliary contacts 2 n/o late make/early break in position 1 1 n/o late make/early break + 1 n/c in position 2 43 33 1T1 | 1T2 | 1T3 | 2T1 | 2T2 | 2T3 22 14 SMD MD 71200 71222 1L1 | 1L2 | 1L3 | 2L1 | 2L2 | 2L3 Switching programme 71222 2 pole with 4 auxiliary contacts 2 n/o late make/early break in position 1 2 n/o late make/early break in position 2 43 1T1 | 1T2 | 1T3 | 2T1 | 2T2 | 2T3 54 64 SMD MF

# Sälzer

### Technical Information Switching diagrams


#### Switching diagrams 71300-71321

# Changeover Switches, 3 pole

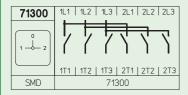


Switching programme 71300

3 pole without auxiliary contacts

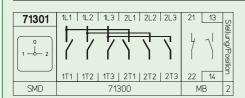


Switching programme 71301

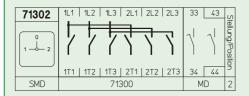- 3 pole with 2 auxiliary contacts
- 1 n/o late make/early break + 1 n/c in position 2




Switching programme 71302

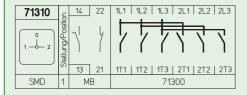- 3 pole with 2 auxiliary contacts
- 2 n/o late make/early break in position 2




Switching programme 71310

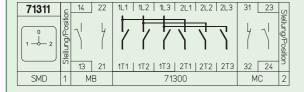- 3 pole with 2 auxiliary contacts
- 1 n/o late make/early break + 1 n/c in position 1




Switching programme 71311

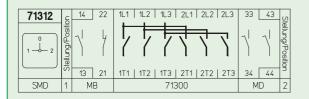- 3 pole with 4 auxiliary contacts
- 1 n/o late make/early break + 1 n/c in position 1
- 1 n/o late make/early break + 1 n/c in position 2




Switching programme 71312

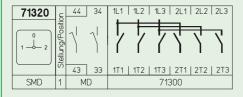- 3 pole with 4 auxiliary contacts
- 1 n/o late make/early break + 1 n/c in position 1
- 2 n/o late make/early break in position 2



Switching programme 71320

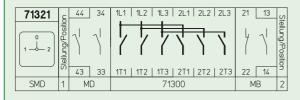- 3 pole with 2 auxiliary contacts
- 2 n/o late make/early break in position 1




Switching programme 71321

- 3 pole with 4 auxiliary contacts
- 2 n/o late make/early break in position 1
- 1 n/o late make/early break + 1 n/c in position 2

# Technical Information Switching diagrams


### Switching diagrams 71322-73500

### Changeover Switches, 3 pole

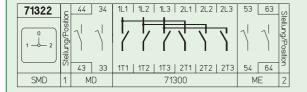


Switching programme 71322 3 pole with 4 auxiliary contacts 2 n/o late make/early break in position 1 2 n/o late make/early break in position 2


# Changeover Switches, 4 pole

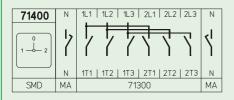

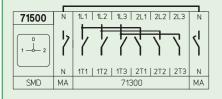Switching programme 71400 4 pole without auxiliary contacts Neutral contact early make/late break




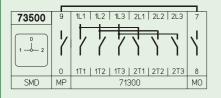Switching programme 71500 4 pole without auxiliary contacts Neutral contact early make/late break neutral jumper




Switching programme 73500 4 pole without auxiliary contacts neutral jumper main contact modules


# Changeover Switches, 3 and 4 pole

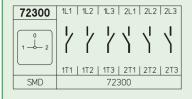

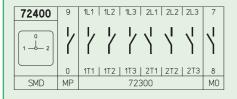Switching programme 72300 3 pole without auxiliary contacts without jumpers



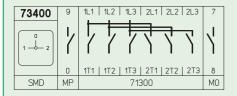Switching programme 72400 4 pole without auxiliary contacts without jumpers



Switching programme 73400 3 pole without auxiliary contacts without neutral jumper main contact modules